

Chapter 31

4. When the switch is open, we have a series LRC circuit involving just the one capacitor near the upper right corner. Equation 31-65 leads to

$$\frac{\omega_d L - \frac{1}{\omega_d C}}{R} = \tan \phi_o = \tan(-20^\circ) = -\tan 20^\circ.$$

Now, when the switch is in position 1, the equivalent capacitance in the circuit is $2C$. In this case, we have

$$\frac{\omega_d L - \frac{1}{2\omega_d C}}{R} = \tan \phi_1 = \tan 10.0^\circ.$$

Finally, with the switch in position 2, the circuit is simply an LC circuit with current amplitude

$$I_2 = \frac{\mathcal{E}_m}{Z_{LC}} = \frac{\mathcal{E}_m}{\sqrt{\left(\omega_d L - \frac{1}{\omega_d C}\right)^2}} = \frac{\mathcal{E}_m}{\frac{1}{\omega_d C} - \omega_d L}$$

where we use the fact that $(\omega_d C)^{-1} > \omega_d L$ in simplifying the square root (this fact is evident from the description of the first situation, when the switch was open). We solve for L , R and C from the three equations above, and the results are as follows:

$$(a) \quad R = \frac{-\mathcal{E}_m}{I_2 \tan \phi_o} = \frac{-120 \text{ V}}{(2.00 \text{ A}) \tan(-20.0^\circ)} = 165 \, \Omega,$$

$$(b) \quad L = \frac{\mathcal{E}_m}{\omega_d I_2} \left(1 - 2 \frac{\tan \phi_1}{\tan \phi_o} \right) = \frac{120 \text{ V}}{2\pi(60.0 \text{ Hz})(2.00 \text{ A})} \left(1 - 2 \frac{\tan 10.0^\circ}{\tan(-20.0^\circ)} \right) = 0.313 \text{ H},$$

(c) and

$$C = \frac{I_2}{2\omega_d \mathcal{E}_m (1 - \tan \phi_1 / \tan \phi_o)} = \frac{2.00 \text{ A}}{2(2\pi)(60.0 \text{ Hz})(120 \text{ V})(1 - \tan 10.0^\circ / \tan(-20.0^\circ))} \\ = 1.49 \times 10^{-5} \text{ F}.$$

6. (a) The rms current is

$$\begin{aligned}
 I_{\text{rms}} &= \frac{\mathcal{E}_{\text{rms}}}{Z} = \frac{\mathcal{E}_{\text{rms}}}{\sqrt{R^2 + (2\pi fL - 1/2\pi fC)^2}} \\
 &= \frac{75.0\text{ V}}{\sqrt{(20.0\ \Omega)^2 + \{2\pi(550\text{ Hz})(25.0\ \text{mH}) - 1/[2\pi(550\ \text{Hz})(4.70\ \mu\text{F})]\}^2}} \\
 &= 2.35\text{ A}.
 \end{aligned}$$

(b) The rms voltage across R is $V_{ab} = I_{\text{rms}}R = (2.35\text{ A})(20.0\ \Omega) = 47.1\text{ V}$.

(c) The rms voltage across C is

$$V_{bc} = I_{\text{rms}}X_C = \frac{I_{\text{rms}}}{2\pi fC} = \frac{2.35\text{ A}}{2\pi(550\text{ Hz})(4.70\ \mu\text{F})} = 144.85\text{ V} \approx 145\text{ V}.$$

(d) The rms voltage across L is

$$V_{cd} = I_{\text{rms}}X_L = 2\pi I_{\text{rms}}fL = 2\pi(2.35\text{ A})(550\text{ Hz})(25.0\text{ mH}) = 203.25\text{ V} \approx 203\text{ V}.$$

(e) The rms voltage across C and L together is

$$V_{bd} = |V_{bc} - V_{cd}| = |144.85\text{ V} - 203.25\text{ V}| = 58.4\text{ V}.$$

(f) The rms voltage across R , C , and L together is

$$V_{ad} = \sqrt{V_{ab}^2 + V_{bd}^2} = \sqrt{(47.1\text{ V})^2 + (58.4\text{ V})^2} = 75.0\text{ V}.$$

(g) For the resistor R , the power dissipated is $P_R = \frac{V_{ab}^2}{R} = \frac{(47.1\text{ V})^2}{20.0\ \Omega} = 111\text{ W}$.

(h) No energy dissipation in C .

(i) No energy dissipation in L .

7. This circuit contains no reactances, so $\mathcal{V}_{\text{rms}} = I_{\text{rms}} R_{\text{total}}$. Using Eq. 31-71, we find the average dissipated power in resistor R is

$$P_R = I_{\text{rms}}^2 R = \left(\frac{\mathcal{V}_{\text{rms}}}{r + R} \right)^2 R.$$

In order to maximize P_R we set the derivative equal to zero:

$$\frac{dP_R}{dR} = \frac{\mathcal{V}_{\text{rms}}^2 \left[(r + R)^2 - 2(r + R)R \right]}{(r + R)^4} = \frac{\mathcal{V}_{\text{rms}}^2 (r - R)}{(r + R)^3} = 0 \Rightarrow R = r$$

18. (a) From Eq. 31-4, we have $L = (\omega^2 C)^{-1} = ((2\pi f)^2 C)^{-1} = 2.41 \mu\text{H}$.

(b) The total energy is the maximum energy on either device (see Fig. 31-4). Thus, we have $U_{\text{max}} = \frac{1}{2} L I^2 = 21.4 \text{ pJ}$.

(c) Of several methods available to do this part, probably the one most “in the spirit” of this problem (considering the energy that was calculated in part (b)) is to appeal to $U_{\text{max}} = \frac{1}{2} Q^2 / C$ (from Chapter 26) to find the maximum charge: $Q = \sqrt{2 C U_{\text{max}}} = 82.2 \text{ nC}$.

42. (a) After the switch is thrown to position b the circuit is an LC circuit. The angular frequency of oscillation is $\omega = 1/\sqrt{LC}$. Consequently,

$$f = \frac{\omega}{2\pi} = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(27.0 \times 10^{-3} \text{ H})(6.20 \times 10^{-6} \text{ F})}} = 389 \text{ Hz}.$$

(b) When the switch is thrown, the capacitor is charged to $V = 34.0 \text{ V}$ and the current is zero. Thus, the maximum charge on the capacitor is

$$Q = VC = (34.0 \text{ V})(6.20 \times 10^{-6} \text{ F}) = 2.11 \times 10^{-4} \text{ C}.$$

The current amplitude is

$$I = \omega Q = 2\pi f Q = 2\pi (389 \text{ Hz})(2.11 \times 10^{-4} \text{ C}) = 0.642 \text{ A}.$$

60. **THINK** We have a series RLC circuit. Since R , L , and C are in series, the same current is driven in all three of them.

EXPRESS The capacitive and the inductive reactances can be written as

$$X_C = \frac{1}{\omega_d C} = \frac{1}{2\pi f_d C}, \quad X_L = \omega_d L = 2\pi f_d L.$$

The impedance of the circuit is $Z = \sqrt{R^2 + (X_L - X_C)^2}$, and the current amplitude is given by $I = \varepsilon_m / Z$.

ANALYZE (a) Substituting the values given, we find the capacitive reactance to be

$$X_C = \frac{1}{2\pi f_d C} = \frac{1}{2\pi(60.0 \text{ Hz})(70.0 \times 10^{-6} \text{ F})} = 37.894 \, \Omega.$$

Similarly, the inductive reactance is

$$X_L = 2\pi f_d L = 2\pi(60.0 \text{ Hz})(230 \times 10^{-3} \text{ H}) = 86.708 \, \Omega.$$

Thus, the impedance is

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(400 \, \Omega)^2 + (37.894 \, \Omega - 86.708 \, \Omega)^2} = 403 \, \Omega.$$

(b) The phase angle is

$$\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right) = \tan^{-1} \left(\frac{86.708 \, \Omega - 37.894 \, \Omega}{400 \, \Omega} \right) = 69.6^\circ.$$

(c) The current amplitude is

$$I = \frac{\varepsilon_m}{Z} = \frac{36.0 \text{ V}}{403 \, \Omega} = 89.3 \text{ mA}.$$

LEARN The circuit in this problem is more inductive since $X_L > X_C$. The phase angle is positive, so the current lags behind the applied emf.