

## Chapter 27

# 28. (a) The batteries are identical and, because they are connected in parallel, the potential differences across them are the same. This means the currents in them are the same. Let  $i$  be the current in either battery and take it to be positive to the left. According to the junction rule the current in  $R$  is  $2i$  and it is positive to the right. The loop rule applied to either loop containing a battery and  $R$  yields

$$\mathcal{E} - ir - 2iR = 0 \Rightarrow i = \frac{\mathcal{E}}{r + 2R}.$$

The power dissipated in  $R$  is

$$P = (2i)^2 R = \frac{4\mathcal{E}^2 R}{(r + 2R)^2}.$$

We find the maximum by setting the derivative with respect to  $R$  equal to zero. The derivative is

$$\frac{dP}{dR} = \frac{4\mathcal{E}^2}{(r + 2R)^3} - \frac{16\mathcal{E}^2 R}{(r + 2R)^3} = \frac{4\mathcal{E}^2 (r - 2R)}{(r + 2R)^3}.$$

The derivative vanishes (and  $P$  is a maximum) if  $R = r/2$ . With  $r = 0.400 \, \Omega$ , we have  $R = 0.200 \, \Omega$ .

(b) We substitute  $R = r/2$  into  $P = 4\mathcal{E}^2 R/(r + 2R)^2$  to obtain

$$P_{\max} = \frac{4\mathcal{E}^2 (r/2)}{[r + 2(r/2)]^2} = \frac{\mathcal{E}^2}{2r} = \frac{(14.0 \, \text{V})^2}{2(0.400 \, \Omega)} = 245 \, \text{W}.$$

# 29. (a) By symmetry, when the two batteries are connected in parallel the current  $i$  going through either one is the same. So from  $\mathcal{E} = ir + (2i)R$  with  $r = 0.400 \, \Omega$  and  $R = 2.00r$ , we get

$$i_R = 2i = \frac{2\mathcal{E}}{r + 2R} = \frac{2(12.0\text{V})}{0.400 \, \Omega + 2(0.800 \, \Omega)} = 12.0 \, \text{A}.$$

(b) When connected in series  $2\mathcal{E} - i_R r - i_R r - i_R R = 0$ , or  $i_R = 2\mathcal{E}/(2r + R)$ . The result is

$$i_R = 2i = \frac{2\mathcal{E}}{2r + R} = \frac{2(12.0 \, \text{V})}{2(0.400 \, \Omega) + 0.800 \, \Omega} = 15.0 \, \text{A}.$$

(c) They are in series arrangement, since  $R > r$ .

(d) If  $R = r/2.00$ , then for parallel connection,

$$i_R = 2i = \frac{2\mathcal{E}}{r + 2R} = \frac{2(12.0\text{V})}{0.400 \, \Omega + 2(0.200 \, \Omega)} = 30.0 \, \text{A}.$$

(e) For series connection, we have

$$i_R = 2i = \frac{2\mathcal{E}}{2r + R} = \frac{2(12.0 \, \text{V})}{2(0.400 \, \Omega) + 0.200 \, \Omega} = 24.0 \, \text{A}.$$

(f) They are in parallel arrangement, since  $R < r$ .

# 30. (a) We note that the  $R_1$  resistors occur in series pairs, contributing net resistance  $2R_1$  in each branch where they appear. Since  $\mathcal{E}_2 = \mathcal{E}_3$  and  $R_2 = 2R_1$ , from symmetry we know that the currents through  $\mathcal{E}_2$  and  $\mathcal{E}_3$  are the same:  $i_2 = i_3 = i$ . Therefore, the current through  $\mathcal{E}_1$  is  $i_1 = 2i$ . Then from  $V_b - V_a = \mathcal{E}_2 - iR_2 = \mathcal{E}_1 + (2R_1)(2i)$  we get

$$i = \frac{\mathcal{E}_2 - \mathcal{E}_1}{4R_1 + R_2} = \frac{5.0\text{ V} - 3.0\text{ V}}{4(2.0\ \Omega) + 4.0\ \Omega} = 0.32\text{ A}.$$

Therefore, the current through  $\mathcal{E}_1$  is  $i_1 = 2i = 0.64\text{ A}$ .

(b) The direction of  $i_1$  is downward.

(c) The current through  $\mathcal{E}_2$  is  $i_2 = 0.32\text{ A}$ .

(d) The direction of  $i_2$  is upward.

(e) From part (a), we have  $i_3 = i_2 = 0.32\text{ A}$ .

(f) The direction of  $i_3$  is also upward.

(g)  $V_a - V_b = -iR_2 + \mathcal{E}_2 = -(0.32\text{ A})(4.0\ \Omega) + 5.0\text{ V} = 2.7\text{ V}$ .

# 35. The current in the circuit is

$$i = (150 \text{ V} - 80 \text{ V}) / (4.0 \, \Omega + 6.0 \, \Omega) = 7.0 \text{ A}.$$

So from  $V_Q + 150 \text{ V} - (6.0 \, \Omega)i = V_P$ , we get

$$V_Q = 100 \text{ V} + (6.0 \, \Omega)(7.0 \text{ A}) - 150 \text{ V} = -8.0 \text{ V}.$$

# 39. In the steady state situation, the capacitor voltage will equal the voltage across  $R_2 = 15 \text{ k}\Omega$ :

$$V_0 = R_2 \frac{\mathcal{E}}{R_1 + R_2} = (15.0 \text{ k}\Omega) \left( \frac{20.0 \text{ V}}{10.0 \text{ k}\Omega + 15.0 \text{ k}\Omega} \right) = 12.0 \text{ V}.$$

Now, multiplying Eq. 27-39 by the capacitance leads to  $V = V_0 e^{-t/RC}$  describing the voltage across the capacitor (and across  $R_2 = 15.0 \text{ k}\Omega$ ) after the switch is opened (at  $t = 0$ ). Thus, with  $t = 0.01400 \text{ s}$ , we obtain

$$V = (12) e^{-0.014 / (15000)(0.4 \times 10^{-6})} = 1.163 \text{ V}.$$

Therefore, using Ohm's law, the current through  $R_2$  is  $1.163/15000 = 7.76 \times 10^{-5} \text{ A}$ .

# 48. First, we note in  $V_4$ , that the voltage across  $R_4$  is equal to the sum of the voltages across  $R_5$  and  $R_6$ :

$$V_4 = i_6(R_5 + R_6) = (2.50 \text{ A})(8.00 \Omega + 4.00 \Omega) = 30.0 \text{ V}.$$

The current through  $R_4$  is then equal to  $i_4 = V_4/R_4 = (30.0 \text{ V})/(16.0 \Omega) = 1.88 \text{ A}$ .

By the junction rule, the current in  $R_2$  is

$$i_2 = i_4 + i_6 = 1.88 \text{ A} + 2.50 \text{ A} = 4.38 \text{ A},$$

so its voltage is  $V_2 = (2.00 \Omega)(4.38 \text{ A}) = 8.75 \text{ V}$ .

The loop rule tells us the voltage across  $R_3$  is  $V_3 = V_2 + V_4 = 38.8 \text{ V}$  (implying that the current through it is  $i_3 = V_3/(2.00 \Omega) = 19.38 \text{ A}$ ).

The junction rule now gives the current in  $R_1$  as

$$i_1 = i_2 + i_3 = 4.38 \text{ A} + 19.38 \text{ A} = 23.8 \text{ A},$$

implying that the voltage across it is  $V_1 = (23.8 \text{ A})(2.00 \Omega) = 47.5 \text{ V}$ . Therefore, by the loop rule,

$$\mathcal{E} = V_1 + V_3 = 47.5 \text{ V} + 38.8 \text{ V} = 86.3 \text{ V}.$$